



Related:



My Maxim



Didn't

Products Overview		^
1-Wire and iButton	Memory	
Amplifiers	Microcontrollers	
Analog Switches and Multiplexers	Military and Aerospace	
Audio	Optical Communications	
Automotive	Power and Battery Management	
Clock Generation and Distribution	Powerline Networking	
Data Converters	Real-Time Clocks	
Design Services and Analog IP Blocks	Sensors and Sensor Interface	
Digital Potentiometers	Supervisors, Voltage Monitors, Sequencers	
Embedded Security	T/E Carrier and Packetized Communications	
Energy-Measurement and Metering SoCs	Video	
Filters (Analog)	Voltage References	
Interface	Wireless and RF	

Parametric Search What's New Patent Marking				Find What You Need?
Solutions Overview				^
Automotive and	Consumer	Computing	Industrial	Military and
Transpo	Electronics	and Storage	Control and	Aerospace
Electric Vehicles	Cell	Desktops and	Automation	Handheld/Portabl
Infotainment	Phone/Smartphon	Servers	Industrial	е
Systems	е	Financial	Power	Satellite Ground
Automotive	Home Video	Terminals	Test and	Suppo
Systems	MP3/Portable	Notebook	Measureme	
	Media Player	Computers	nt	
Communication	Tablets	Storage		
				Building Block

s and Net Cable Infrastructure Datacom Optical Networking Telecom Wireless Infrastructure Wireless Network	Wireless Handheld	Energy Generation Distribution Consumption Communication s	Monit Home Medic Medic Imagi	nostics, corin e cal cal	Advisor Analog S Chain Power Architect FPGA Po	Signal
Related: Analog Integration Microsite Design						Didn't Find What You Need?
Overview Technical	Design Tools,	Packaging and		Part Sele	ection	Design for
Documents	Models, Software	Reliability		Paramet		FPGAs
Application	Modeling/Simulation	Packaging		Search	iiC	Technical
Notes	EE-Sim	Information		Part Num	nher	Support
Reference	CAD and Layout	Packaging Outlin	ne	Search	ibei	Free
Design Center	Evaluation Kits	Drawings		What's N	lew/	Samples
Tutorials	Power-Supply	Land Pattern		Cross-		EE
Product Guides	Cookbook	Drawings		Reference	ce.	Glossary
Solutions	Applications	QA and Reliabilit	tv	Search		EE-Mail
Guides	Software	Information	-9	Part Sele	ection	Newsletter
Brochures User Guides and Manuals Product Videos Demo Videos Data Sheets	Calculators	Environmental Management and Materials Information (EMMI) Lead-Free/RoHS Lookup Topmark Code	6	Advice		

Lookup

Didn't Find What You Need?

Buy Direct Price and Availability Search <u>S</u>earch

Order Online Free Samples **Prototypes** Order by Phone Order by Fax or Email

Sales and Distribution Worldwide Sales

Distributors

View Order Offices Status Worldwide My Franchised Account **Distributors** Contact Authorized Us End-of-Life

Surplus

Customer

Service

Semiconductor

Equipment

Front-End Fab Equipment **Back-End Test**

Equipment

Didn't Find What You Need?

Support

Website

Issues

Index of Support **Options**



Maxim

Products

Customer Service

North America 888-Maxim-IC (888-629-4642) salesus@maximintegrated.com **Europe** + 353 (0) 1 223 5500 saleseurope@maximintegrated.com

Asia and Oceania

+ 886-2-8770-5666

sales-asia@maximintegrated.com sales-japan@maximintegrated.com sales-korea@maximintegrated.com sales-

australia@maximintegrated.com sales-

newzealand@maximintegrated.com

Didn't Find

What You Need?

About Ho			Neeu:
About Us Overview Our Values	Maxim at a Glance	Quick Facts	^
Investor Relations Careers	At Maxim, we invent highly integrated solutions that make technology	President and CEO Tunç Doluca	NASDAQ MXIM
Corporate Responsibility Partnerships with	seamless. We channel our collective expertise to stretch the limits of technology, understand your needs, and help you	Headquarters San Jose, CA,	Employees 9300
Suppliers Worldwide Locations Leadership Newsroom	get to market faster. Financial Strength \$2.4 billion (approx.) revenue in FY2013 \$585 million revenue in Q1 FY2014	Founded 1983. We celebrate our 30th anniversary in 2013.	
Awards Contact Us	\$3.76 billion in assets in Q1 FY2014 \$1.03 billion in cash in Q1 FY2014	Detailed Profile Corporate Infographic (PDF)	

Career Opportunities

My Maxim Home

Related:

My Home Shopping
Identity Free
MailBox Samples
Subscriptions Buy Online
Interests Order
Footprints Status

Didn't Find What You Need?

Didn't Find

What You Need?

Maxim > Design Support > Technical Documents > Tutorials > A/D and D/A Conversion/Sampling Circuits > APP 1080 Keywords: sar,successive approximation,adc,analog to digital,converter,precision Related Parts

Share

Understanding SAR ADCs: Their Architecture and Comparison with Other ADCs

Oct 02, 2001

Abstract: Successive-approximation-register (SAR) analog-to-digital converters (ADCs) represent the majority of the ADC market for medium- to high-resolution ADCs. SAR ADCs provide up to 5Msps sampling rates with resolutions from 8 to 18 bits. The SAR architecture allows for high-performance, low-power ADCs to be packaged in small form factors for today's demanding applications.

This paper will explain how the SAR ADC operates by using a binary search algorithm to converge on the input signal. It also explains the heart of the SAR ADC, the capacitive DAC, and the high-speed comparator. Finally, the article will contrast the SAR architecture with pipeline, flash, and sigma-delta ADCs.

Introduction

Successive-approximation-register (SAR) analog-to-digital converters (ADCs) are frequently the architecture of choice for medium-to-high-resolution applications with sample rates under 5 megasamples per second (Msps). Resolution for SAR ADCs most commonly ranges from 8 to 16 bits, and they provide low power consumption as well as a small form factor. This combination of features makes these ADCs ideal for a wide variety of applications, such as portable/battery-powered instruments, pen digitizers, industrial controls, and data/signal acquisition.

As the name implies, the SAR ADC basically implements a binary search algorithm. Therefore, while the internal circuitry may be running at several megahertz (MHz), the ADC sample rate is a fraction of that number due to the successive-approximation algorithm.

SAR ADC Architecture

Although there are many variations for implementing a SAR ADC, the basic architecture is quite simple (see **Figure 1**). The analog input voltage (V_{IN}) is held on a track/hold. To implement the binary search algorithm, the N-bit register is first set to midscale (that is, 100... .00, where the MSB is set to 1). This forces the DAC output (V_{DAC}) to be $V_{REF}/2$, where V_{REF} is the reference voltage provided to the ADC. A comparison is then performed to determine if V_{IN} is less than, or greater than, V_{DAC} . If V_{IN} is greater than V_{DAC} , the comparator output is a logic high, or 1, and the MSB of the N-bit register remains at 1. Conversely, if V_{IN} is less than V_{DAC} , the comparator output is a logic low and the MSB of the register is cleared to logic 0. The SAR control logic then moves to the next bit down, forces that bit high, and does another comparison. The sequence continues all the way down to the LSB. Once this is done, the conversion is complete and the N-bit digital word is available in the register.

Share on email Email

More Sharing ServicesOther Channels

More

Download, PDF Format (54kB)
Related Parts/Samples
Sign-Up for EE-Mail™
Print

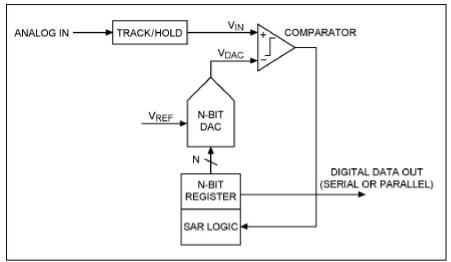


Figure 1. Simplified N-bit SAR ADC architecture.

Figure 2 shows an example of a 4-bit conversion. The y-axis (and the bold line in the figure) represents the DAC output voltage. In the example, the first comparison shows that $V_{IN} < V_{DAC}$. Thus, bit 3 is set to 0. The DAC is then set to 0100_2 and the second comparison is performed. As $V_{IN} > V_{DAC}$, bit 2 remains at 1. The DAC is then set to 0110_2 , and the third comparison is performed. Bit 1 is set to 0, and the DAC is then set to 0101_2 for the final comparison. Finally, bit 0 remains at 1 because $V_{IN} > V_{DAC}$.

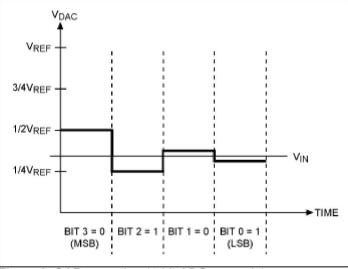


Figure 2. SAR operation (4-bit ADC example).

Notice that four comparison periods are required for a 4-bit ADC. Generally speaking, an N-bit SAR ADC will require N comparison periods and will not be ready for the next conversion until the current one is complete. This explains why these ADCs are power- and space-efficient, yet are rarely seen in speed-and-resolution combinations beyond a few mega-samples per second (Msps) at 14 to 16 bits. Some of the smallest ADCs available on the market are based on the SAR architecture. The MAX1115/MAX1116 and MAX1117/MAX1118 8-bit ADCs and their higher resolution counterparts, the MAX1086 and the MAX1286 (10 and 12 bits, respectively), fit in tiny SOT23 packages measuring 3mm x 3mm. The 12-bit MAX11102 comes in a 3mm x 3mm TDFN package or a 3mm x 5mm μ MAX® package.

There is another notable feature of SAR ADCs: power dissipation scales with the sample rate. This contrasts with flash or pipelined ADCs which usually have constant power dissipation versus sample rate. This scaled power dissipation is especially useful in low-power applications or applications where the data acquisition is not

continuous (for example, PDA digitizers).

In-Depth SAR Analysis

The two critical components of a SAR ADC are the comparator and the DAC. As we shall see later, the track/hold shown in Figure 1 can be embedded in the DAC and, therefore, may not be an explicit circuit.

A SAR ADC's speed is limited by:

The settling time of the DAC, which must settle to within the resolution of the overall converter, for example, $\frac{1}{2}$ LSB

The comparator, which must resolve small differences in V_{IN} and V_{DAC} within the specified time

The logic overhead

The DAC

The maximum settling time of the DAC is usually determined by its MSB settling. This is simply because the MSB transition represents the largest excursion of the DAC output. In addition, the linearity of the overall ADC is limited by the linearity of the DAC. Therefore, because of the inherent component-matching limitaions, SAR ADCs with more than 12 bits of resolution will often require some form of trimming or calibration to achieve the necessary linearity. Although it is somewhat process-and-design-dependent, component matching limits the linearity to about 12 bits in practical DAC designs.

Many SAR ADCs use a capacitive DAC that provides an inherent track/hold function. Capacitive DACs employ the principle of charge redistribution to generate an analog output voltage. Because these types of DACs are prevalent in SAR ADCs, it is beneficial to discuss their operation.

A capacitive DAC consists of an array of N capacitors with binary weighted values plus one "dummy LSB" capacitor. Figure 3 shows an example of a 16-bit capacitive DAC connected to a comparator. During the acquisition phase, the array's common terminal (the terminal at which all the capacitors share a connection, see Figure 3) is connected to ground and all free terminals are connected to the input signal (analog in or V_{IN}). After acquisition, the common terminal is disconnected from ground and the free terminals are disconnected from V_{IN} , thus effectively trapping a charge proportional to the input voltage on the capacitor array. The free terminals of all the capacitors are then connected to ground, driving the common terminal negative to a voltage equal to $-V_{\text{IN}}$.

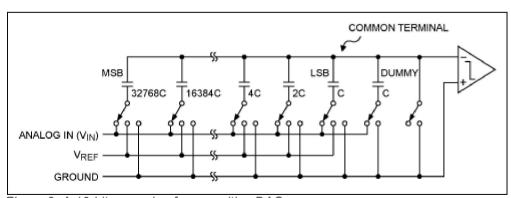


Figure 3. A 16-bit example of a capacitive DAC.

As the first step in the binary search algorithm, the bottom plate of the MSB capacitor is disconnected from ground and connected to V_{REF} . This drives the common terminal in the positive direction by an amount equal to $\frac{1}{2}V_{REF}$.

Therefore, $V_{COMMON} = -V_{IN} + \frac{1}{2} \times V_{REF}$

The comparator output yields a logic 1 if V_{COMMON} < 0 (i.e., V_{IN} > $\frac{1}{2}$ × V_{REF}). The comparator output yields logic 0 if V_{IN} < $\frac{1}{2}$ × V_{REF} .

If the comparator output is logic 1, then the bottom plate of the MSB capacitor stays connected to V_{REF} . Otherwise, the bottom plate of the MSB capacitor is connected back to ground.

The bottom plate of the next smaller capacitor is then connected to V_{REF} and the new V_{COMMON} voltage is compared with ground.

This continues until all the bits have been determined.

In general, V_{COMMON} = - V_{IN} + B_{N-1} × V_{REF} /2 + B_{N-2} × V_{REF} /4 + B_{N-1} × V_{REF} /8 + ... + B0 × V_{RFF} /2 (B_ comparator output/ADC output bits).

DAC Calibration

In an ideal DAC, each of the capacitors associated with the data bits would be exactly twice the value of the next-smaller capacitor. In high-resolution ADCs (for example, 16 bits), this results in a range of values too wide to be realized in an economically feasible size. The 16-bit SAR ADCs like the MAX195 use a capacitor array that actually consists of two arrays capacitively coupled to reduce the LSB array's effective value. The capacitors in the MSB array are production trimmed to reduce errors. Small variations in the LSB capacitors contribute insignificant errors to the 16-bit result. Unfortunately, trimming alone does not yield 16-bit performance or compensate for changes in performance due to changes in temperature, supply voltage, and other parameters. For this reason, the MAX195 includes a calibration DAC for each capacitor in the MSB array. These DACs are capacitively coupled to the main DAC output and offset the main DAC's output according to the value on their digital inputs.

During calibration, the correct digital code to compensate for the error in each MSB capacitor is determined and stored. Thereafter, the stored code is provided to the appropriate calibration DAC whenever the corresponding bit in the main DAC is high. This compensates for errors in the associated capacitor. Calibration is usually initiated by the user or done automatically on power-up. To reduce the effects of noise, each calibration experiment is performed many times (about 14,000 clock cycles in the MAX195), and the results are averaged. Calibration is best performed when the power-supply voltages are stable. High-resolution ADCs should be recalibrated any time that there is a significant change in supply voltages, temperature, reference voltage, or clock characteristics, because these parameters affect the DC offset. If linearity is the only concern, much larger changes in these parameters can be tolerated. Because the calibration data is stored digitally, there is no need to perform frequent conversions to maintain accuracy.

The Comparator

The requirements of the comparator are speed and accuracy. Comparator offset does not affect overall linearity as it appears as an offset in the overall transfer characteristic. In addition, offset-cancellation techniques are usually applied to reduce the comparator offset. Noise, however, is a concern, and the comparator is usually designed to have input-referred noise less than 1 LSB. Additionally, the comparator needs to resolve voltages within the accuracy of the overall system. It needs to be as accurate as the overall system.

SAR ADCs Compared with Other ADC Architectures

Versus Pipelined ADCs

A pipelined ADC employs a parallel structure in which each stage works on 1 to a few bits (of successive samples) concurrently. This inherent parallelism increases throughput, but at a trade-off of power consumption and latency. Latency in this case is defined as the difference between the time when an analog sample is acquired by the ADC and the time when the digital data is available at the output. For example, a five-stage pipelined ADC will have at least five clock cycles of latency, whereas a SAR has only one clock cycle of latency. Note that the latency definition applies only to the throughput of the ADC, not the internal clock of a SAR which runs at many times the frequency of the throughput. Pipelined ADCs frequently have digital error-correction logic to reduce the accuracy requirement of the flash ADCs (i.e., comparators) in each pipeline stage. However, a SAR ADC requires the comparator to be as accurate as the overall system. A pipelined ADC generally requires significantly more silicon area than an equivalent SAR. Like a SAR, a pipelined ADC with more than 12 bits of accuracy usually requires some form of trimming or calibration.

Versus Flash ADCs

A flash ADC is comprised of a large bank of comparators, each consisting of wideband, low-gain preamp(s) followed by a latch. The preamps must only provide gain but do not need to be linear or accurate. This means that only the comparators' trip points have to be accurate. As a result, a flash ADC is the fastest architecture available.

The primary trade-off between a flash ADC's speed is the SAR ADC's significantly lower power consumption and smaller form factor. While extremely fast 8-bit flash ADCs (or their folding/interpolation variants) exist with sampling rates as high as 1.5Gsps (e.g., the MAX104, MAX106, and MAX108), it is much harder to find a 10-bit flash ADC. Moreover, 12-bit (and above) flash ADCs are not commercially viable products. This is simply because the number of comparators in a flash ADC increases by a factor of two for every extra bit of resolution. Meanwhile, each comparator must be twice as accurate. In a SAR ADC, however, the increased resolution requires more accurate components, yet the complexity does not increase exponentially. Of course, SAR ADCs are not capable of the speeds of flash ADCs.

Versus Sigma-Delta Converters

Traditional oversampling/sigma-delta converters used in digital audio applications have limited bandwidths of about 22kHz. Recently, some high-bandwidth sigma-delta converters reached bandwidths of 1MHz to 2MHz with 12 to 16 bits of resolution. These are usually very-high-order sigma-delta modulators (for example, 4th-order or higher), incorporating a multibit ADC and multibit feedback DAC. Sigma-delta converters have the innate advantage over SAR ADCs: they require no special trimming or calibration, even to attain 16 to 18 bits of resolution. Because their sampling rate is much higher than the effective bandwidth, they also do not require anti-alias filters with steep rolloffs at the analog inputs. The backend digital filters take care of this. The oversampling nature of the sigma-delta converter can also tend to "average out" any system noise at the analog inputs.

Sigma-delta converters trade speed for resolution. The need to sample many times (at least 16 times and often more) to produce one final sample dictates that the internal analog components in the sigma-delta modulator operate much faster than the final data rate. The digital decimation filter is also a challenge to design and consumes considerable silicon area. The fastest high-resolution sigma-delta converters are not expected to have significantly higher bandwidth than a few MHz in the near future.

Conclusion

In summary, the primary advantages of SAR ADCs are low power consumption, high resolution and accuracy, and a small form factor. Because of these benefits, SAR ADCs can often be integrated with other larger functions. The main limitations of the SAR architecture are the lower sampling rates and the requirements that the building

blocks, the DAC and the comparator, be as accurate as the overall system.

References

Razavi, Behzad; *Principles of Data Conversion System Design;* IEEE Press, 1995. Van De Plassche, Rudy; *Integrated Analog-to-Digital and Digital-to-Analog Converters;* Kluwer Academic Publishers, 1994.

Maxim Integrated; Understanding Pipelined ADCs.

Baker, R. Jacob, Li, Harry W., Boyce, David E., *CMOS Circuit Design, Layout, and Simulation*, 1st Edition (IEEE Press Series on Microelectronic Systems).

μMAX is a registered trademark of Maxim Integrated Products, Inc.

	Power, 14-Bit Analog-to-Digital Converters	Free Samples
	Parallel Interface	
	Power, 14-Bit Analog-to-Digital Converters Parallel Interface	Free Samples
MAX11102 2Ms ADC	ps/3Msps, Low-Power, Serial 12-/10-/8-Bit	Free Samples
MAX1111 +2.7 ADC	V, Low-Power, Multichannel, Serial, 8-Bit	Free Samples
_	le-Supply, Low-Power, 2-Channel, Serial 8- DCs	Free Samples
	it ADC, 200ksps, 5V Single-Supply with erence	Free Samples
	it ADC, 200ksps, 5V Single-Supply with erence	Free Samples
MAX1162 16-B	it, +5V, 200ksps ADC with 10µA Shutdown	Free Samples
	Power, 16-Bit Analog-to-Digital Converters Parallel Interface	Free Samples
	Power, 16-Bit Analog-to-Digital Converters Parallel Interface	Free Samples
Char	sps/300ksps, Single-Supply, Low-Power, 8- nnel, Serial 12-Bit ADCs with Internal erence	Free Samples
	sps, +5V, 8-/4-Channel, 12-Bit ADCs with V Reference and Parallel Interface	Free Samples
MAX195 16-B	it, 85ksps ADC with 10µA Shutdown	Free Samples

Next Steps	
FF-Mail	Subscribe to FF-Mail and receive automatic notice of new documents

in your areas of interest.

Download Download, PDF Format (54kB)

Share More Sharing ServicesOther Channels Share on email Email this

page to an associate or friend.

APP 1080: Oct 02, 2001

TUTORIAL 1080, AN1080, AN 1080, APP1080, Appnote1080, Appnote 1080

© 2014 Maxim Integrated

